
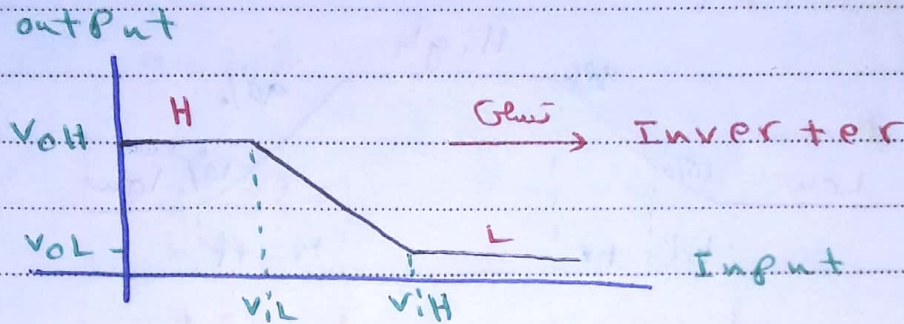


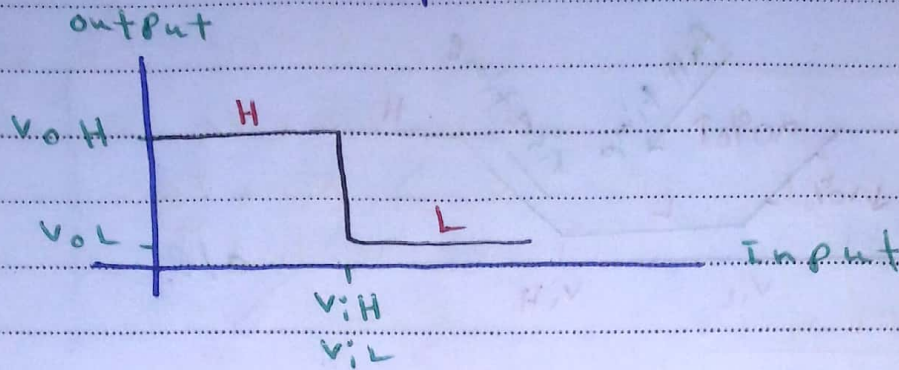Subject: الالكترونيات رقميّة / Digital Electronics



Voltage Input Low Input أقل من V_{IL} H. V_{IL}

VTC: Voltage Transfer characteristics

logic swing $V_{LS} = V_{OH} - V_{OL}$

transition width $= V_{TW} = V_{IH} - V_{IL}$

*** Noise margin:**

$$V_{NMH} = V_{OH} - V_{IH}$$



$$V_{NML} = V_{IL} - V_{OL}$$

*** Noise Immunity**

$$V_{NIH} = \frac{V_{NMH}}{V_{LS}}$$

$$V_{NIL} = \frac{V_{NML}}{V_{LS}}$$

Subject:

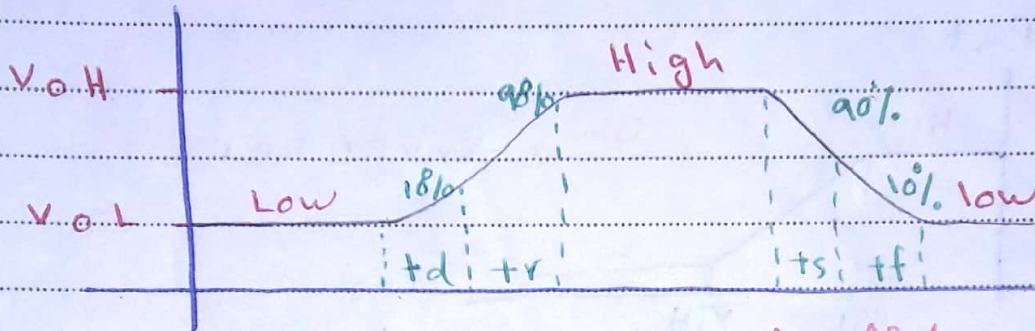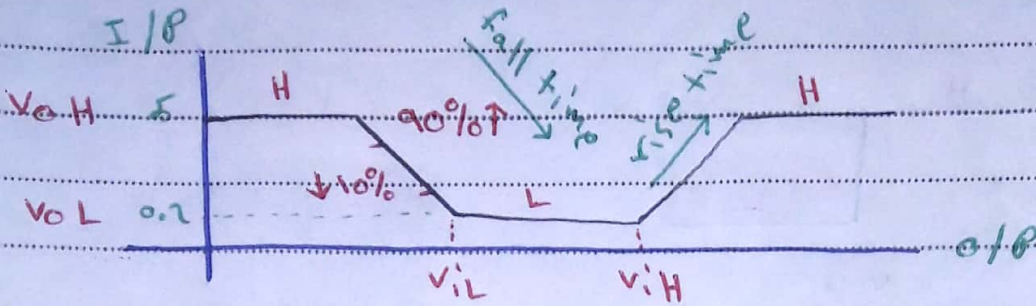

$$t_{on} = t_d + t_r$$

$$t_{off} = t_s + t_f$$


t_d : delay time

t_s : rise time


t_s : storage time

t_f : fall time

OR - gate

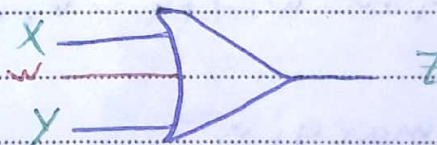

X	Y	Z
L	L	L
L	H	H
H	L	H
H	H	H

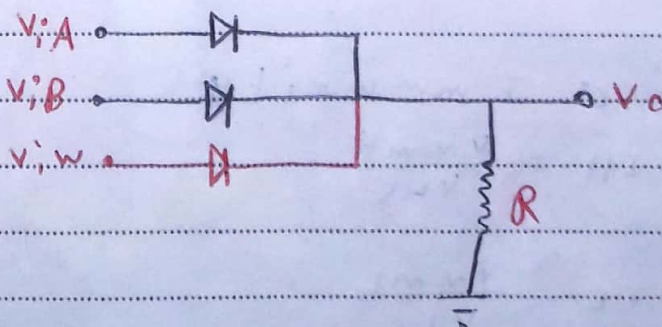

V_OA	V_OB	V_O
L	L	L
L	H	H
H	L	H
H	H	H


$$H V_O = V_{iB} - 0.7$$

$$H V_O = V_{iA} - 0.7$$

$$L: V < 0.7$$

$$H: V > 0.7$$

Subject:


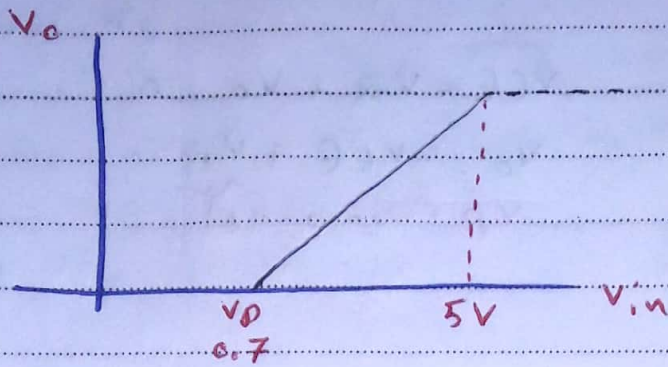


$$L: V < 0.7$$



$$H: V > 0.7$$

AND - gate

X	Y	Z
L	L	L
L	H	L
H	L	L
H	H	H

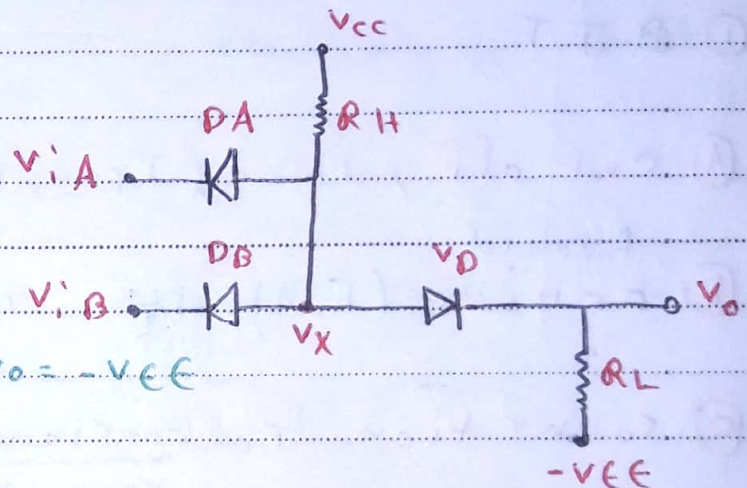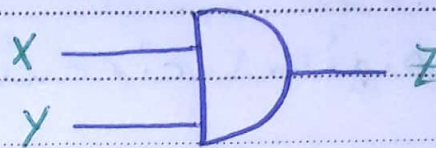

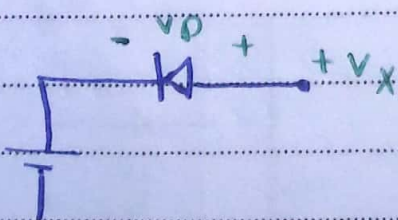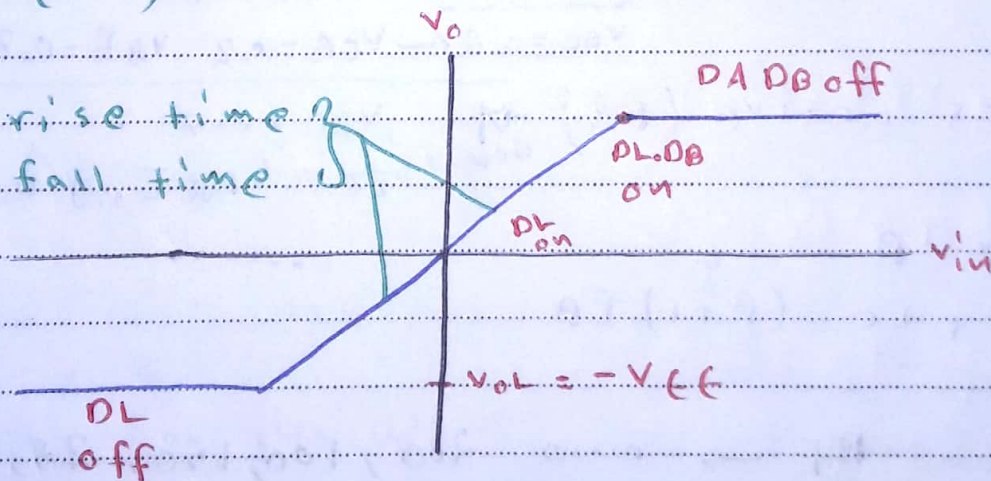* DL (open) off $\Rightarrow V_o = -V_{EE}$
DL (on)




$$V_X = V_i + V_{DB}$$

$$V_o = V_X - V_{OL}$$

$$V_o = V_i + V_{DB} - V_{OL}$$

$$V_o = V_i$$

Subject:

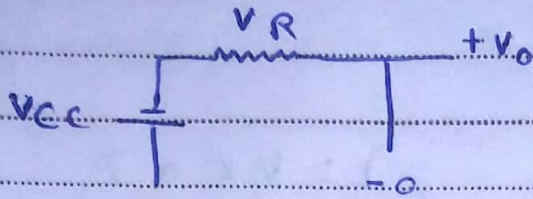

$$V_{CE} - V_R + V_O = 0$$


$$V_O = -V_{CE} + V_R$$

V_R $\rightarrow$ $\frac{V_{CC} - V_O}{R_H + R_L}$

$$I = \frac{V_{CC} - V_{OL} + V_{EC}}{R_H + R_L}$$

ch 4 digital circuit

① BJT

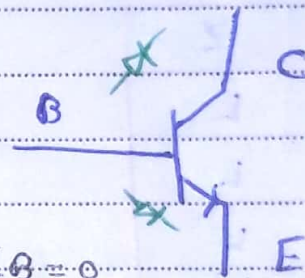

① cut off, $I_C = 0$, $I_E = 0$, $I_B = 0$

② ^{forward} active (F.A) $\rightarrow$ $V_{BE} = 0.7$

③ saturation $I_C = \text{constant} = \beta B_F I_B$ $I_B \uparrow$ $I_E \uparrow$
 $V_{BC} = 0.6 \leftarrow V_{CE} = 0.2$ $V_{BE} = 0.8 V$

④ Reverse active (RA) $\rightarrow$ $V_{BC} = 0.7$ $I_E = -\beta_R I_B$ $\beta_R \approx \beta_F$

$$I_C = \beta_F I_B$$


$$I_E = I_B + I_C = (\beta + 1) I_B$$

$0 < \beta < 1$ $\beta_F \rightarrow \text{range } 200, 100, 150, 25, 50$

$\beta_R \rightarrow \approx 1$ range

Subject:

find V_{CE1}

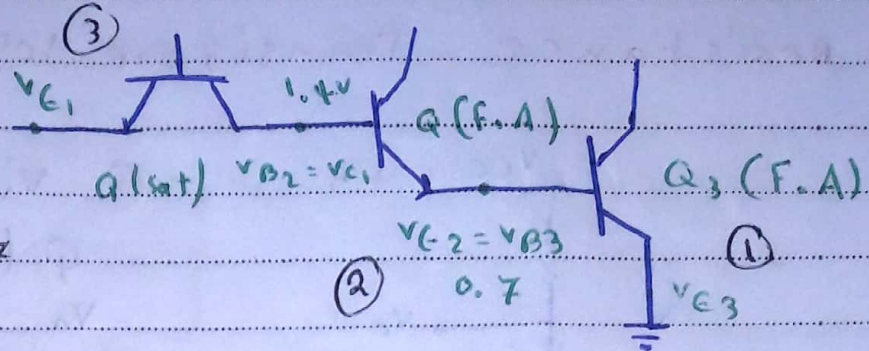

① $V_{BE3} = 0.7$

$V_{B3} - V_{E3} = 0.7$

$V_{B3} = 0.7$

② $V_{BE2} = 0.7$

$V_{B2} = 0.7 + V_{E2}$

$V_{B2} = 0.7 + 0.7 = 1.4V$

③ $V_{CE1} = 0.2$

$V_{C1} - V_{E1} = 0.2$

$V_{E1} = V_{C1} - 0.2$


$V_{E1} = 1.4 - 0.2 = 1.2V$

find I

$I_B \rightarrow \mu A \rightarrow$ directly load

$$I = \frac{V_{CC} - 2V_D}{R_1 + R_2 + R_3}$$


find V_{XB}

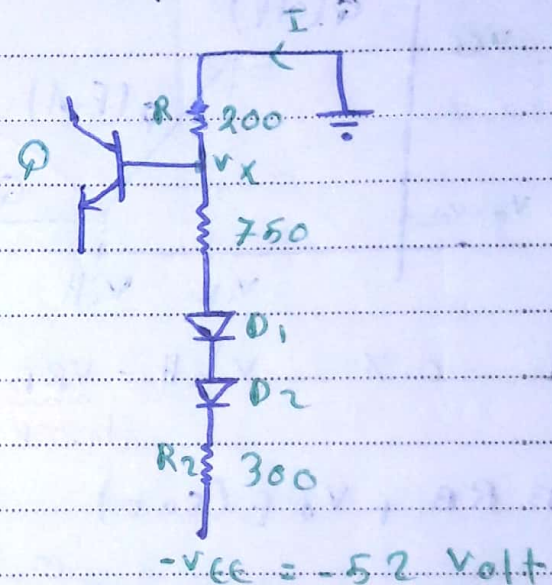


Design family

1. power Dissipation

2. fan-out

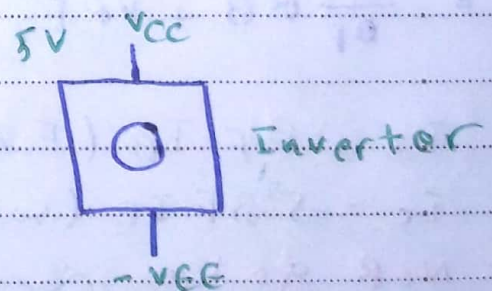

تیا، قلیل اس فیمل
تیا، علی اس فیمل

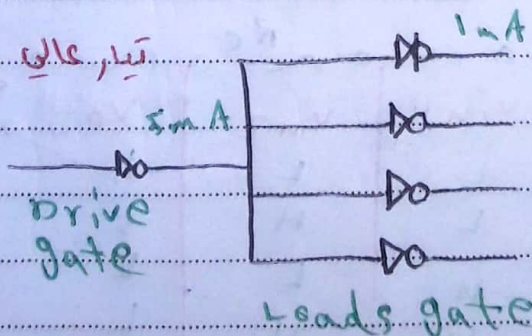


fan-out: loads gates
drive gate

Subject:


/ /

Resistance - Transistor logic (RTL)

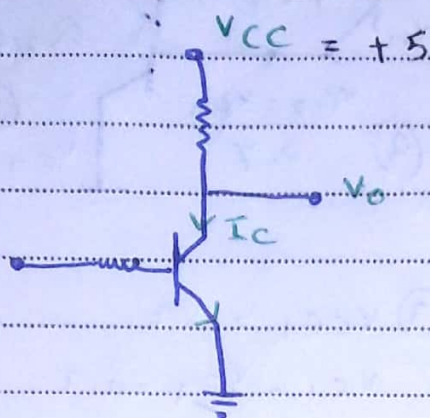


① V_{in} Low
 Q (off)
 $V_o = V_{CC}$ (V_{oH})

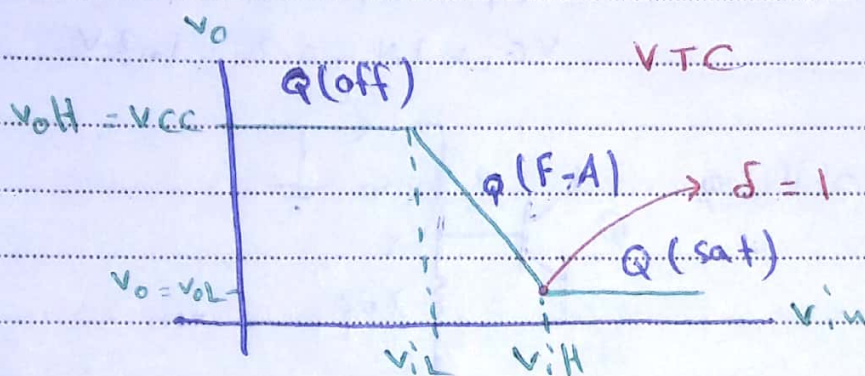② V_{in} High
 Q (sat)
 $V_o = V_{CE(sat)} = 0.2$



✓ Will be ✓
 Inverter

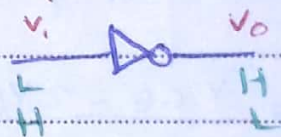

$$V_{inL} = 0.7 \quad V_{inH} = \underbrace{V_{RB}}_{\text{drop } V(sat)} + V_{RE(sat)}$$


$$= I_B R_B + V_{RE(sat)}$$

$$= \frac{I_C}{\beta_F} R_B + V_{RE(sat)} \quad \text{0.8}$$

$$I_C = \beta_F I_B (F.A)$$

$$I_C = \beta_F I_B (sat) \quad = \quad \underline{I_C = V_{CC} - V_{CE(sat)}} \quad R_C$$

NOR gate

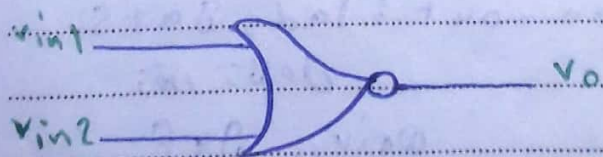

V_{in1}	V_{in2}	V_o
L	L	H
L	H	L
H	L	L
H	H	L

S

T

A


R

S Notebook


Subject:.....

L: off (Q)

H: sat (Q)

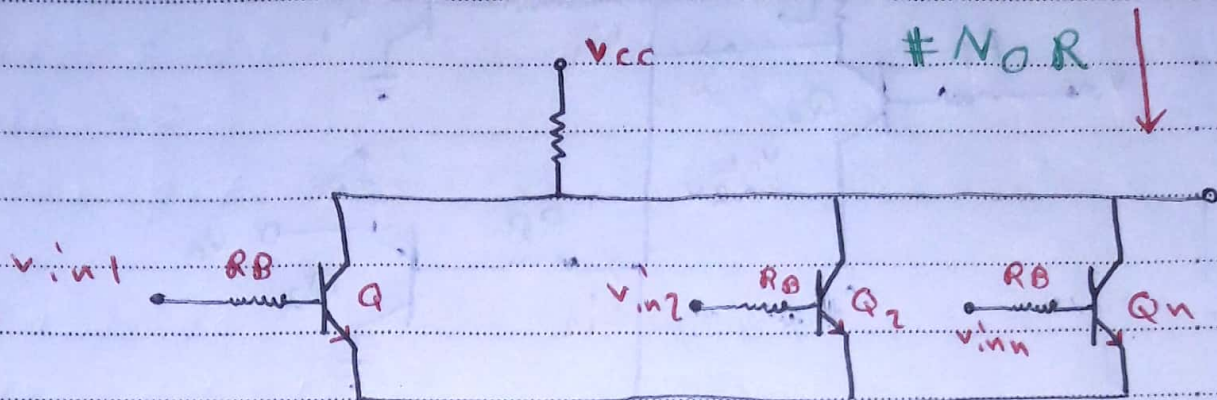


NAND gate

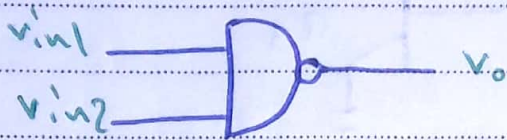

v_{in1}	v_{in2}	v_o
L	L	H
H	L	H
L	H	H
H	H	L

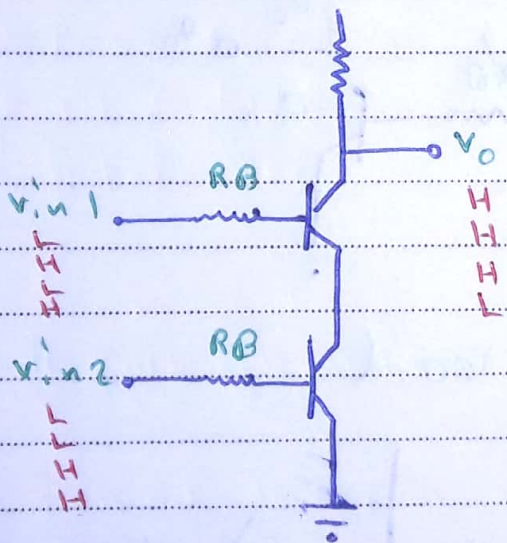Not 0, 1 > 1, 1 > 1, 1, 1: Note
AND gate chesi vo 1, 1, 1




$$V_c = (V_{CE1} + V_{CE2})_{sat} = 0.2 + 0.2 = 0.4$$

$$V_o = \sum_{n=1}^N 0.2 = 0.2 \times N$$

Subject:

Sample / /

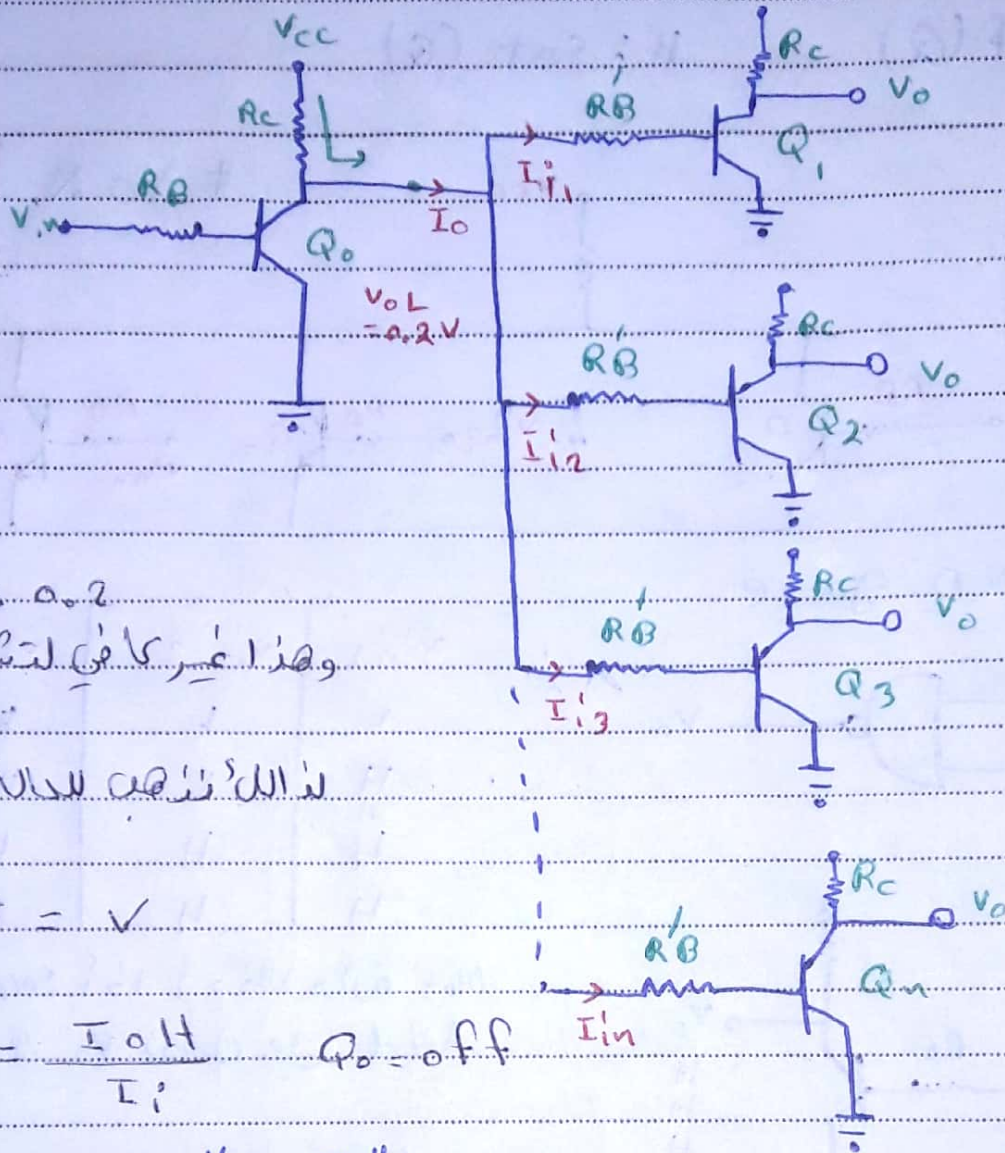

①

$$V_{OL} = 0.2$$

প্রতিটি এমিটার ওল্ট, এমিটার

(H) এর অর্থ হল

②

$$V_{OH} = V$$

$$N = \frac{I_{OH}}{I_i} \quad Q_0 = \text{off}$$

$$I_{OH} = I_{RC} = \frac{V_{CC} - V_{OH}}{R_C}$$


$$I_i = I_{RB} = \frac{V_{OH} - V_{BE(sat)}}{R'_B}$$

$$V_{OH} = V_{iHmin} = I'_B R'_B + V_{BE(sat)}$$

$$= \frac{I'_C}{\beta_F} R'_B + V_{BE(sat)}$$

$$V_{OH} = V_{iHmin} = \frac{V_{CC} - V_{CE(sat)}}{\beta_F R_C} \cdot R'_B + V_{BE(sat)}$$

load

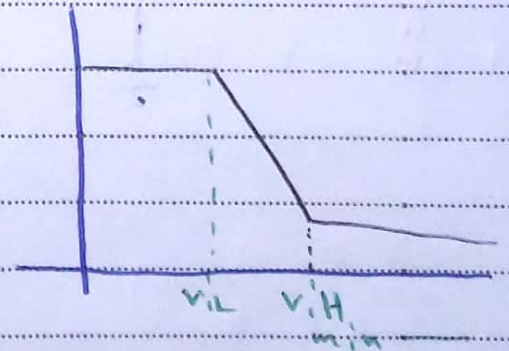

Subject:

/ /

$$R_B = 10K \Omega$$

$$R_C = 1K \Omega$$

$$V_{CC} = 5V$$

$$\beta_f = 25$$

$$V_{OH} = \frac{5 - 0.2}{25 \cdot 1K} \cdot 10K + 0.8 = 2.7V$$

$$I_{OH} = \frac{5 - 2.7}{1K} = 2.3mA$$

$$I_i = \frac{2.7 - 0.8}{10K} = 0.19mA$$

$$N = \frac{I_o}{I_i} = \frac{2.3mA}{0.19mA} = 12.19 = 12$$