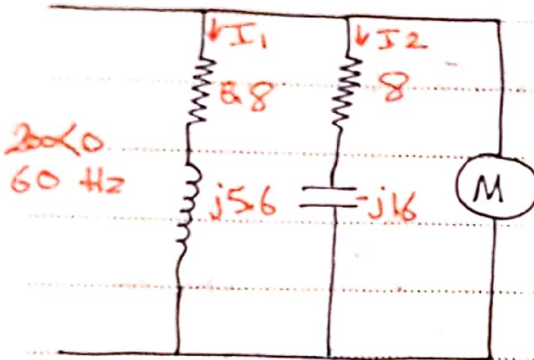


Example (Quiz) :-



$S_3 = 5 \text{ kVA at } 0.8 \text{ pf lag}$

$$1) S = \frac{|V|^2}{Z_1^*} = \frac{|200|^2}{0.8 - j5.6} = \underbrace{1000}_{\text{W}} + \underbrace{j7000}_{\text{var}}$$


$$S_2 = \frac{(200)^2}{8 + j0.16} = \underbrace{1000}_{\text{W}} - \underbrace{j2000}_{\text{var}}$$

$$S = 5000 \angle 36.87^\circ = 4000 + j2000$$

$$\therefore S_{\text{Total}} = S_1 + S_2 + S_3 = 6 + j8 = 10 \angle 53.13^\circ$$

$$2) S = V \cdot I^* \rightarrow I = \frac{S^*}{V} = \frac{1000 \angle -53.3^\circ}{200 \angle 0^\circ} = 50 \angle -53.13^\circ \text{ A}$$

lag -
lead +

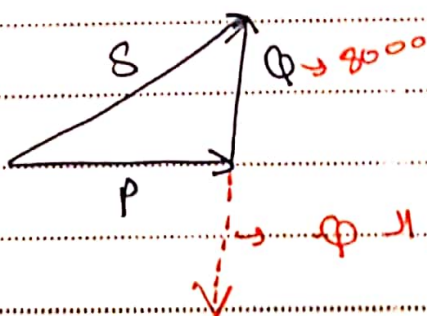

سبجی

Subject :

3 / 3 / 2019

$$\therefore Z_c = \frac{|V|^2}{S_c^*} = \frac{200^2}{j5000} = -j5 \Omega$$

$$\therefore C = \frac{1}{2\pi \cdot 60.5} = \frac{10^6}{2\pi \cdot 60.5} = 530.5 \mu F$$

*

*

*

chapter 2 قوا و توان

$$* \text{ average } = \text{ real } = \text{ active power } \rightarrow P = |V||I| \cos \theta$$

$$* \text{ apperant power } = |V||I| \rightarrow \text{ Voltampere (VA)}$$


$$* \text{ reactive power } = Q = |V||I| \sin \theta \rightarrow \text{ VAR}$$

$$* \text{ Complex power } = S = VI^* = P + jQ$$

$$S = \frac{|V|^2}{Z^*}$$


$$* Z = \frac{|V|^2}{S^*}$$

$$* C = \frac{10^6}{2\pi(f) X_c} \rightarrow X_c = \frac{|V|^2}{S_c^*}$$

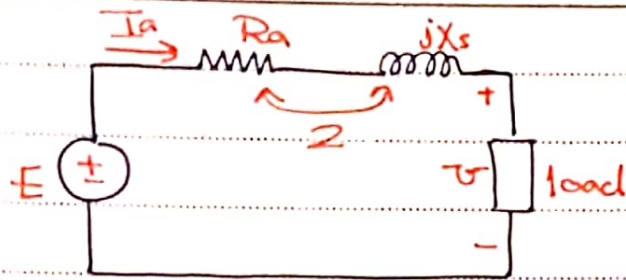

$$\rightarrow E = V_{load} + (I_a \cdot Z_s)$$
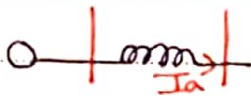
$$\left\{ \begin{array}{l} E < V \\ V < 0 \\ Z_s < 0 \end{array} \right\}$$




$$\rightarrow * E = 4.44 * k.w * f * N \phi$$

$$\rightarrow * f = \frac{P}{2} \cdot \frac{n}{60} = \frac{Pn}{120}$$


$$\rightarrow * V = E - I_a \cdot Z$$

$$\rightarrow * S_{3\phi} = 3 V I_a^*$$


1) $pf = 1$:-

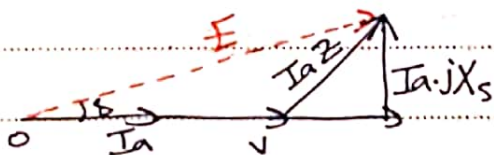

2) pf lag :-

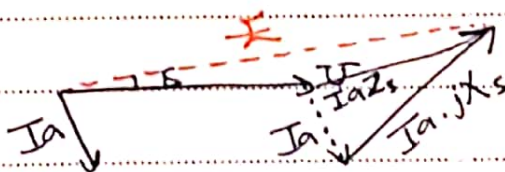

3) pf lead :-

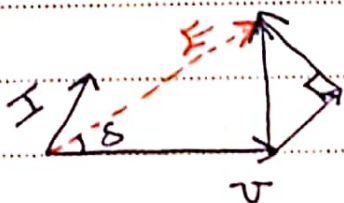

Subject :

3 / 3 / 2019

* Voltage regulation :-

الافتراق في الجهد

$$VR = \frac{U_{no.L} - U_{rated}}{U_{rated}}$$

$$S_{3\phi} = 3 U I_a^*$$

$$I_a = \frac{E \angle \delta - U \angle 0}{Z \angle \alpha}$$

$$S_{3\phi} = \frac{3 |E| |U|}{|Z_s|} \angle \alpha - \delta - \frac{3 |U|^2}{|Z_s|} \angle \alpha$$

$$\therefore P_{3\phi} = \frac{3 |E| |U|}{|Z_s|} \cos \angle \alpha - \delta - \frac{3 |U|^2}{|Z_s|} \angle \alpha$$

$$\therefore Q_{3\phi} = \frac{3 |E| |U|}{|Z_s|} \sin \angle \alpha - \delta - \frac{3 |U|^2}{|Z_s|} \sin \angle 90$$



$$\therefore P_{3\phi \max} = \frac{3 |E| |U|}{X_s} \sin \angle 90$$

$$\therefore P_{3\phi \max} = \frac{3 |E| |U|}{X_s}$$


Ex: (3.1) :-

$$E = I_a (R_a + jX_s) + V_{load}$$


$$E = I_a Z_s + V_{load}$$

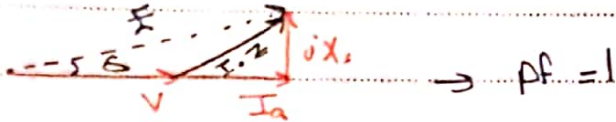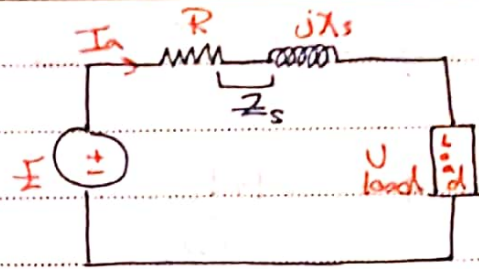

→ pf = 1

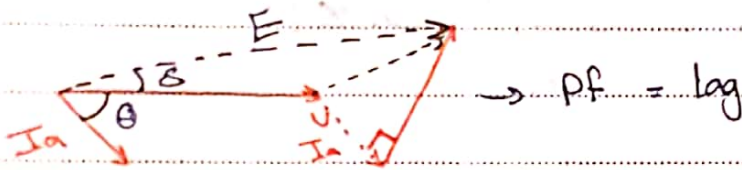

→ pf = lag

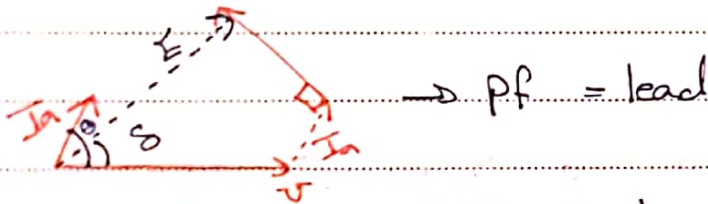

→ pf = lead

Note :- θ الزاوية بين V, I و δ الزاوية بين E, V

* at no load $\Rightarrow I_a = \text{zero}, E = V$

$$E < \delta$$

$$V < 0$$

$$Z < \delta$$

* إذا ما حدد في سؤال ال phase
بتنقل على line

Solution :-

$$S_{3\phi} = 3 V I_a^*$$

$$|E| \angle \delta = |V| \angle 0 + I_a |Z_s| \angle \phi$$

$$\therefore I_a = \frac{|E| \angle \delta - |V| \angle 0}{|Z_s| \angle \phi}$$

$$\therefore S_{3\phi} = 3V I_a^* \rightarrow I_a \text{ في } 200 \text{ V}$$

$$S_{3\phi} = \frac{3|E||V| \angle \delta}{|Z_s|} - \frac{3|V|^2 \angle \delta}{|Z_s|}$$

$$\therefore P_{3\phi} = \frac{3|E||V| \cos \angle \delta}{Z_s} - \frac{3|V|^2 \cos \delta}{|Z_s|} \rightarrow \text{let } \delta = 90^\circ$$

active

$$\therefore Q_{3\phi} = \frac{3|E||V| \sin \angle \delta}{Z_s} - \frac{3|V|^2 \sin \delta}{|Z_s|}$$

$$\therefore \text{active power} = \frac{3|E||V| \sin \delta}{|Z_s|}$$

$$\therefore P_{\max 3\phi} = \frac{3|E||V|}{Z_s} = \sin \delta \rightarrow \delta = 90^\circ \text{ max}$$

ملاحظة: إذا ما كان بالخط V phase يغير الجهد (V line) ويحول إلى V phase عن طريق $\sqrt{3}$ (de power)

Ex (3.1) :-

$$\text{pf} = 0.8 \text{ lag} \rightarrow \cos^{-1}(\text{pf}) = 36.87^\circ \rightarrow \text{lag} \therefore \angle -36.87$$

$$\therefore 50 \angle -36.87 = 40 + j30$$

$$I_a = \frac{S^*}{3V^*} = \frac{(50 \angle -36.87)(10^6)}{3(17.32 \times 10^3 \angle 0)} = 962.25 \angle -36.87 \text{ A}$$

V_{phase}

$$\begin{aligned} E &= V + I_a \cdot jZ_s \\ &= 17.32 \angle 0 + (96225 \angle -36.87^\circ \cdot j9) = 23.558 \angle 17.1^\circ \text{ kV} \end{aligned}$$

$$2) \rho_{\text{max}} = \frac{3|E||V|}{|X_s|} \sin \delta$$

$$25 \text{ MW} = \frac{3|E||V|}{|X_s|} \sin \delta$$

$$\therefore \delta = \sin^{-1} \left(\frac{9.25}{3 \times 23.56 \times 17.32} \right) = 10.591^\circ$$

$$\begin{aligned} I_a &= \frac{E \angle \delta - V \angle 0}{jX_s} = \frac{23.558 \angle 10.591^\circ - 17.32 \angle 0}{j9} \\ &= 807.48 \angle -53.4^\circ \end{aligned}$$

Problem (3.2)