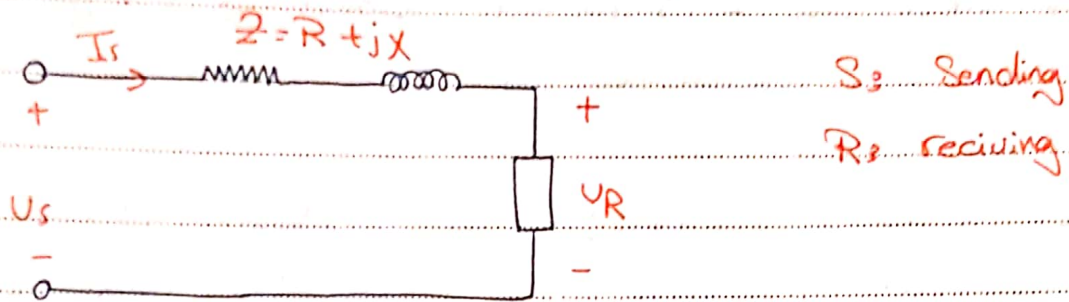





* $V_S = V_R + (I_R \times Z)$ in short circuit:-
 * $I_S = I_R$
 $\rightarrow A=1, B=Z, C=0, D=1$

* $I_s = I_R$

Transmission line 3

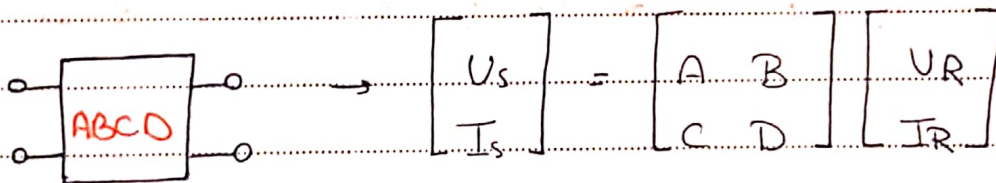- 1) short < 80
- 2) medium $\rightarrow 80 - 250$
- 3) long > 250



$$U_S = AUR + B\bar{I}R$$

$$\therefore T_s = C_{VR} + D_{IR}$$

تطبيق لكل الأنواع $\Rightarrow$ قاعدة عامة $\rightarrow AD - BC = 1$

* at no load $I_R = \text{zero}$

Subject :

31 / 3 / 2019

$$\rightarrow * UR = \frac{U_R(\text{no load}) - U_R(\text{full load})}{U_R(\text{full load})} \times 100\% \rightarrow \text{voltage regulation}$$

$$U_{\text{no load}} = \frac{U_s}{A} \rightarrow A \neq 1 \rightarrow \text{short-circuit } A=1$$

$U_s = U_{R, \text{load}} = U_R$
بقي قابض 4 الحذف "

$$\hookrightarrow * \text{Regulation at short} = \frac{U_s - U_R}{U_R}$$

$$* \text{Regulation in general} = \frac{\frac{U_s}{a} - U_R}{U_R}$$

$$* \eta = \frac{P_{3\phi R}}{P_{3\phi S}} = \frac{I_R \cdot U_R}{I_s \cdot U_s}$$

power factor at load is 1.2 = 20% *

Example :-

220 kV, 40 km, $R = 0.15 \Omega/\text{km}$, $1.3263 \text{ mH}/\text{km}$, $f = 50$

231 Q2 100

lag

a) 381 MVA at 0.8 pf at 220 kV

b) 381 MVA at 0.8 pf leading at 220 kV


Solution :-

$$R = 0.15 \times 40 \text{ km} = 6 \Omega/\text{km}$$

$$XL = (2\pi fL) \cdot L = 0.5 \times 40 \text{ km}$$

$$= 20 \Omega$$

$$Z = (6 + j20) \Omega$$

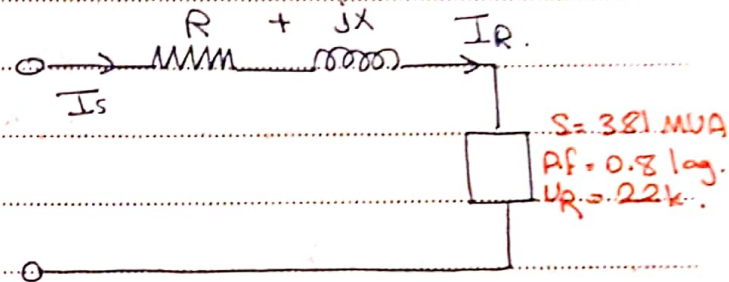

$$V_R/\text{phase} = \frac{220}{\sqrt{3}} = 127 \text{ kV} = 127 \angle 0^\circ \text{ kV}$$

$$I_R = \frac{S_R^*}{3 V_R^*} \Rightarrow S_R = 381 \angle \cos^{-1} 0.8 = 381 \angle -36.87^\circ \text{ MVA}$$

$$\therefore I_R = \frac{381 \angle -36.87^\circ}{3 \times 127 \angle 0^\circ} = 1000 \angle -36.87^\circ$$

$$\therefore V_s/\text{phase} = V_R + (I_R \times Z)$$

$$= 144.33 \angle 4.93^\circ \text{ kV}$$

$$\therefore V_s(\text{L.L.}) = 144.33 \angle 4.93^\circ \times \sqrt{3} = 250 \text{ kV}$$

$$\therefore V_R = \frac{250 - 220}{220} \times 100\% = 13.6\%$$

6 0.799 jlt lag 9.2

active power receiving no jlt active power sending Lilo is

Subject :

31 / 3 / 2019.

(Receiving) $\leftarrow 304.8 = 381 \times 0.8 \leftarrow$ active power $\rightarrow$ grid $\rightarrow$

$3VI^* \leftarrow (3)(1)(144.33) =$ Sending power $\rightarrow$

$\eta = \frac{P_{3\phi R}}{P_{3\phi S}} = \frac{304.8}{322.75} \rightarrow S = 3VI^*$

$= \frac{304.8}{322.75} = 94.4\%$

$\hookrightarrow S_{3\phi} = 3VI^*$

2) $Z = 6 + j20 \Omega$

S at leading pf = 0.8 = $381 \angle -36.87^\circ$ MVA

$\therefore I_R = 1000 \angle -36.87^\circ$ A

$U_S = U_R + I_R \cdot Z = 121.4 \angle 9.29^\circ$ kV

$U_S(L) = 210.26$ kV

$\therefore U_R = \frac{210.26 - 220}{220} \times 100\% = -4.4\%$

Calculation of line drop

$S = (3)(121.4 \angle 9.29^\circ) \cdot (1000 \angle -36.87^\circ \times 10^3)$

$= 322.79 \angle -27.58^\circ$ MVA

load plus

$322.79 \angle +28.79^\circ$

استهلاك